
Morse Tutor Simplified Schematic

A 'port' of the W8BH 'Blue Pill' Morse Tutor to a Mega 2560 by Ken, KM4NFQ "Not Fully Qualified" 6 August 2019 modified by GM4CID to simplify assembly 14 August 2019

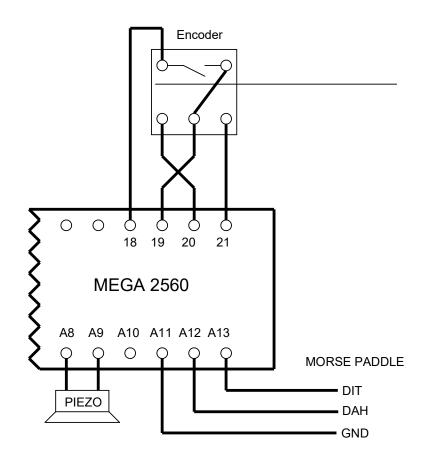Hardware
Arduino Mega 2560
2.4 inch LCD Display Shield
Switched Rotary Encoder
Piezo Sounder



2.4 inch LCD Display Shield mounts directly on Mega 2560

See next page for three wire adds on rear of Mega board

Mega is 5v USB powered from a mobile phone power bank

Wire adds on rear of Mega 2560 board

50 (MISO) to 12 51 (MOSI) to 11 52 (SCK) to 13

Noter - 11, 12 and 13 are set high impedance in sketch

<u>Wire adds are on track side of board, following</u> picture is of the component side.

